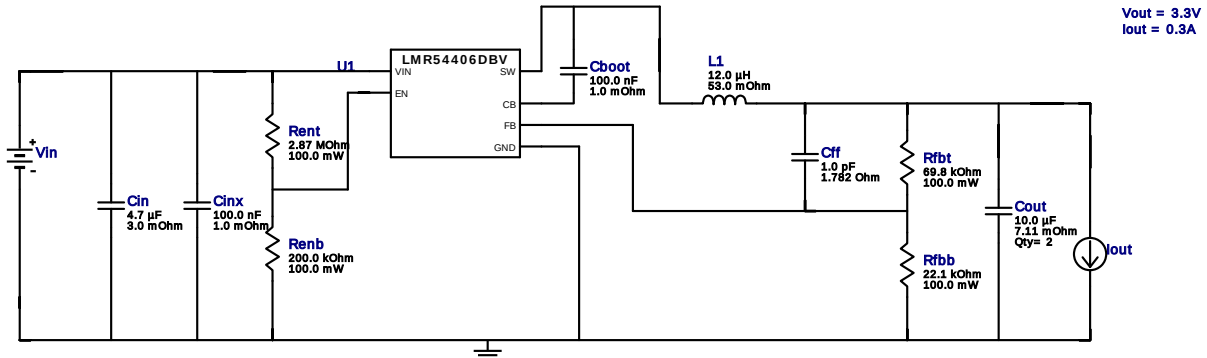


WEBENCH® Design Report







Design : 11 LMR54406DBVR
LMR54406DBVR 6V-36V to 3.30V @ 0.5A















Electrical BOM




Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cboot	Kemet	C0603C104M4RACTU Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0603 5 mm ²
Cff	AVX	06035A1R0CAT2A Series= C0G/NP0	Cap= 1.0 pF ESR= 1.782 Ohm VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0603 5 mm ²
Cin	MuRata	GRM31CR71H475KA12L Series= X7R	Cap= 4.7 uF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 4.98 A	1	\$0.10	 1206 11 mm ²
Cinx	MuRata	GRM188R72A104KA35D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 100.0 V IRMS= 3.85 A	1	\$0.04	 0603 5 mm ²
Cout	Taiyo Yuden	MSASJ219JB5106KTNA01 Series= X5R	Cap= 10.0 uF ESR= 7.11 mOhm VDC= 6.3 V IRMS= 2.7429 A	2	\$0.03	 0805 7 mm ²
L1	Bourns	SRR6038-120Y	L= 12.0 uH 53.0 mOhm	1	\$0.39	 SRR6038 77 mm ²
Renb	Vishay-Dale	CRCW0603200KFKEA Series= CRCW..e3	Res= 200.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
Rent	Vishay-Dale	CRCW06032M87FKEA Series= CRCW..e3	Res= 2.87 MOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
Rfbb	Yageo	RC0603FR-0722K1L Series= ?	Res= 22.1 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
Rfbb	Yageo	RC0603FR-0769K8L Series= ?	Res= 69.8 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
U1	Texas Instruments	LMR54406DBVR	Switcher	1	\$0.47	 DBV0006A 15 mm ²

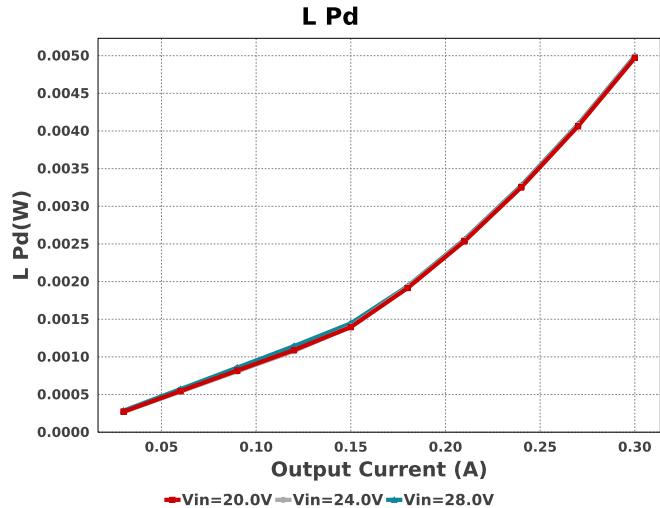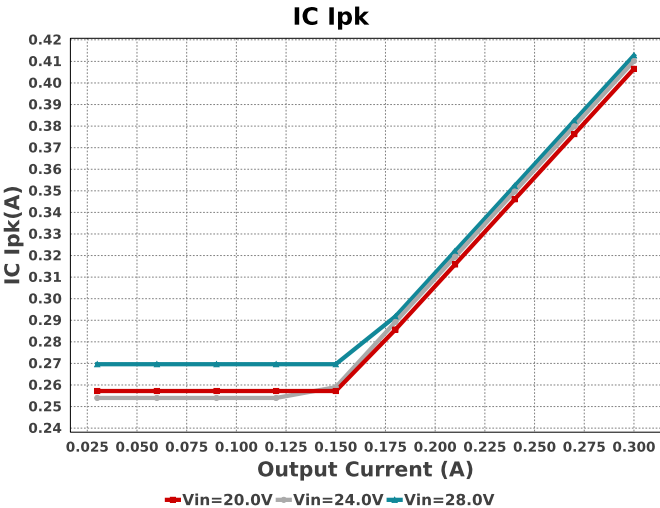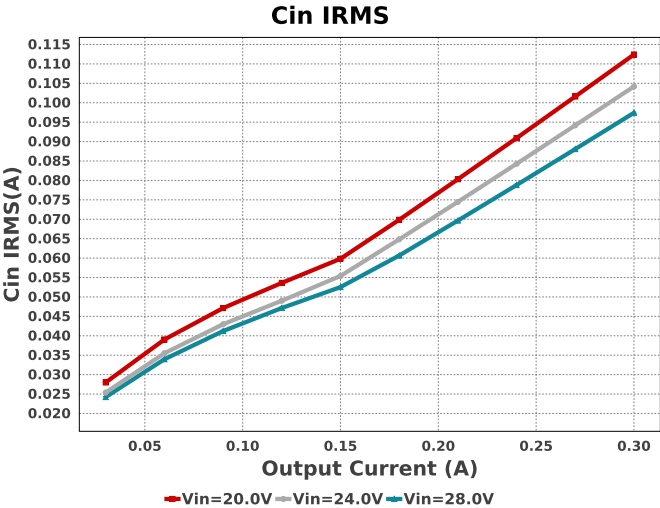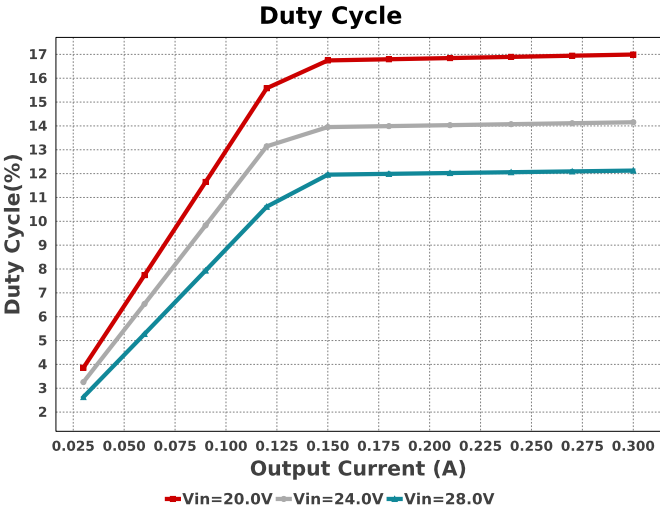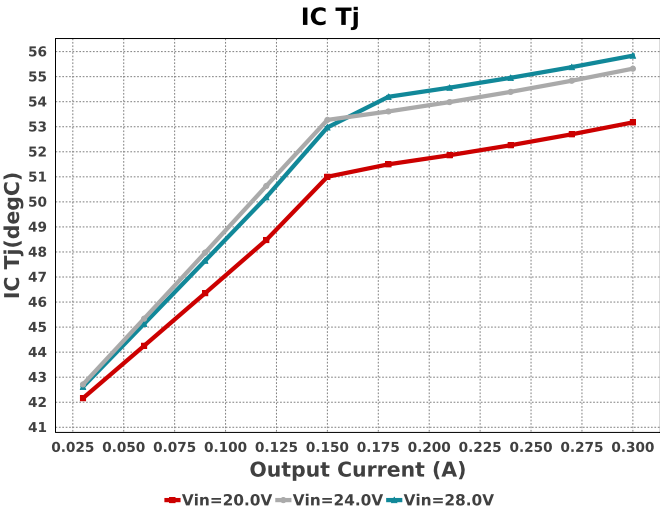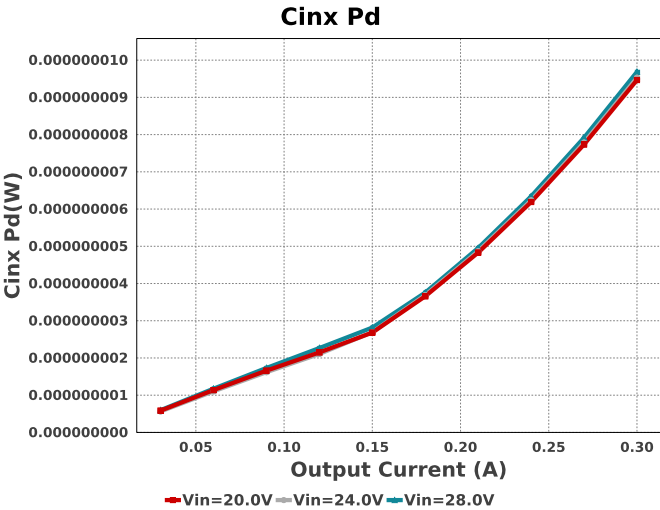

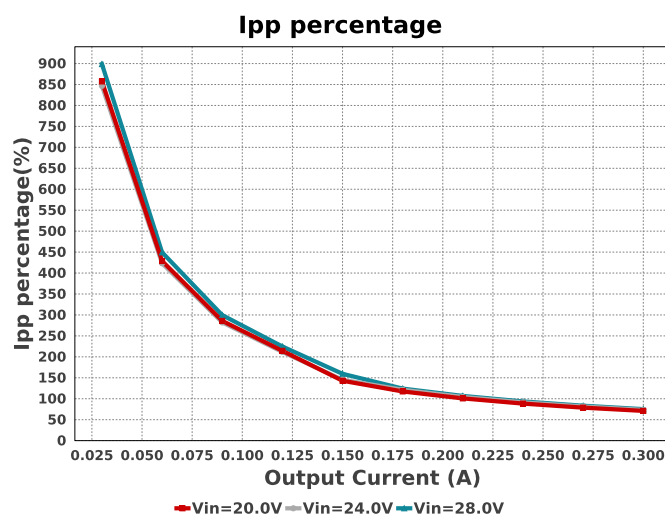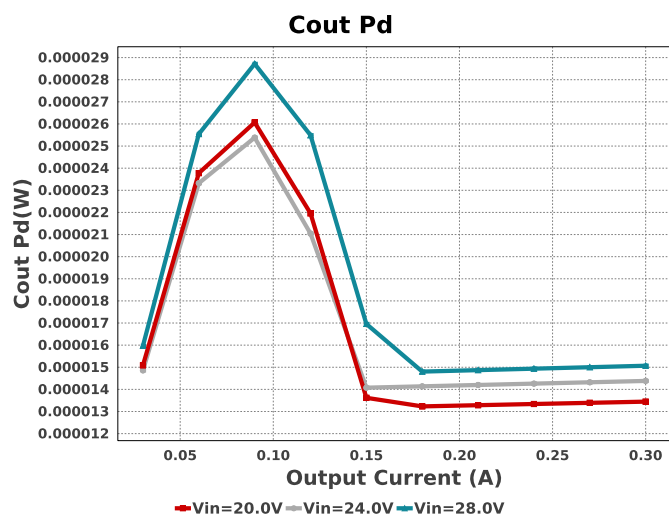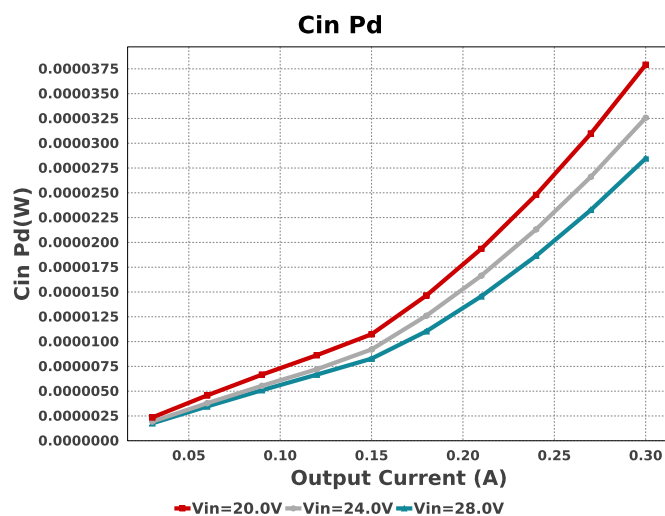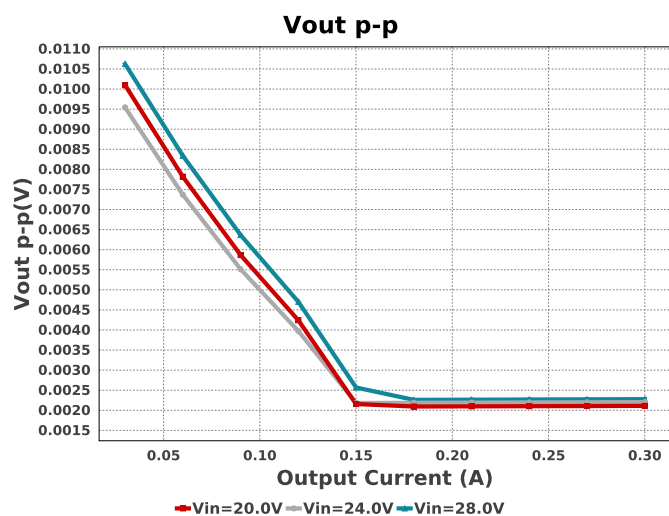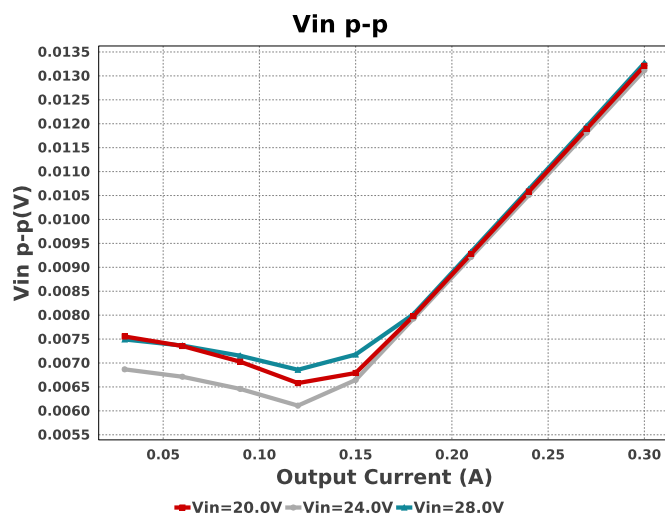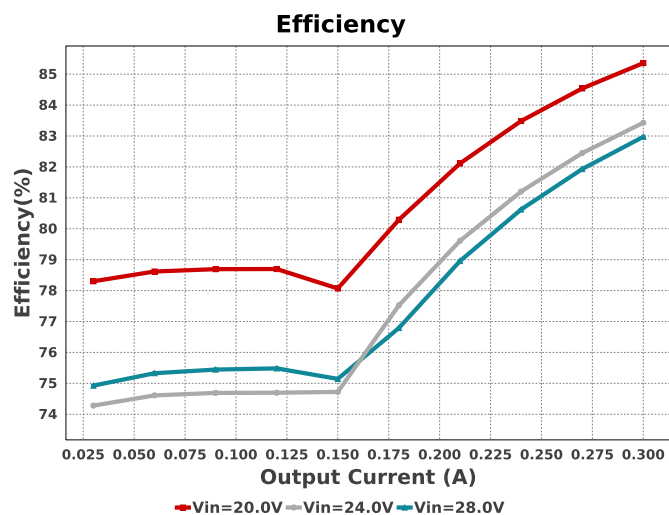

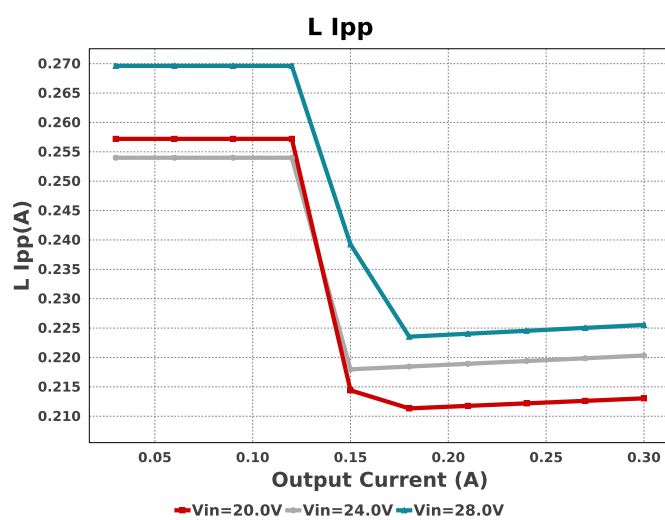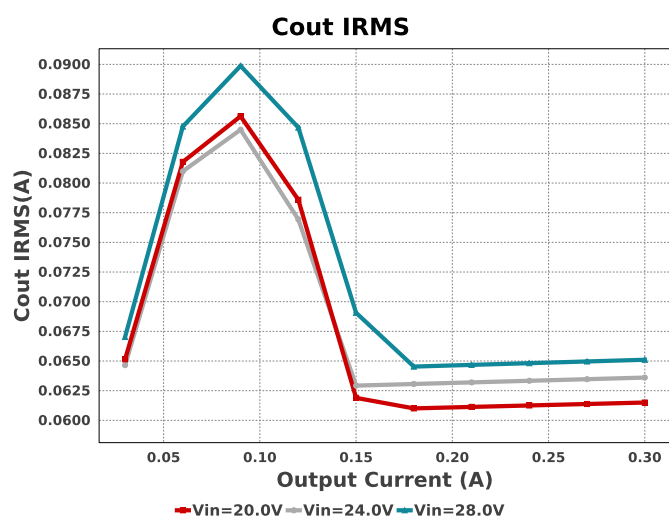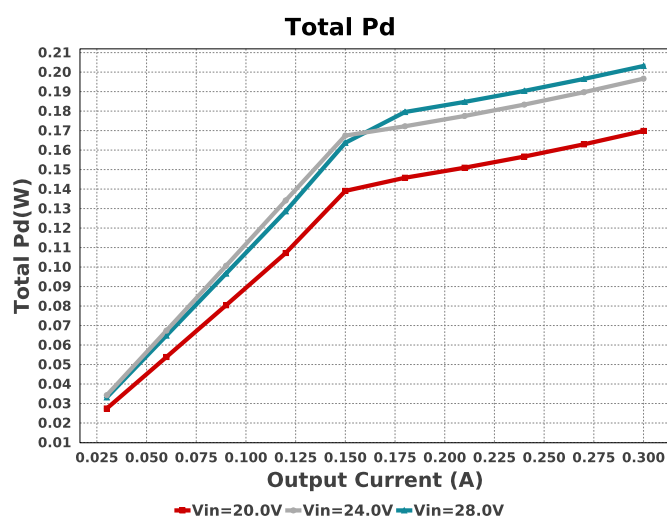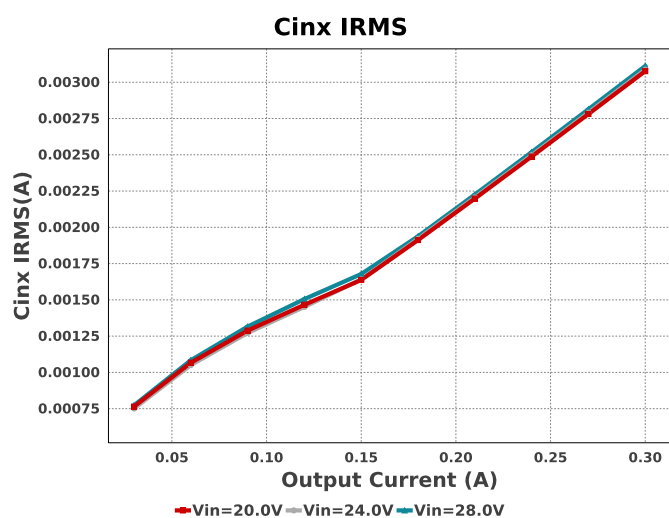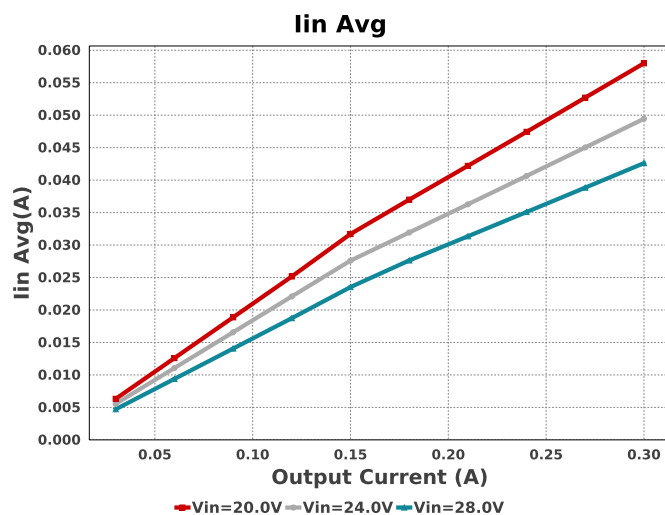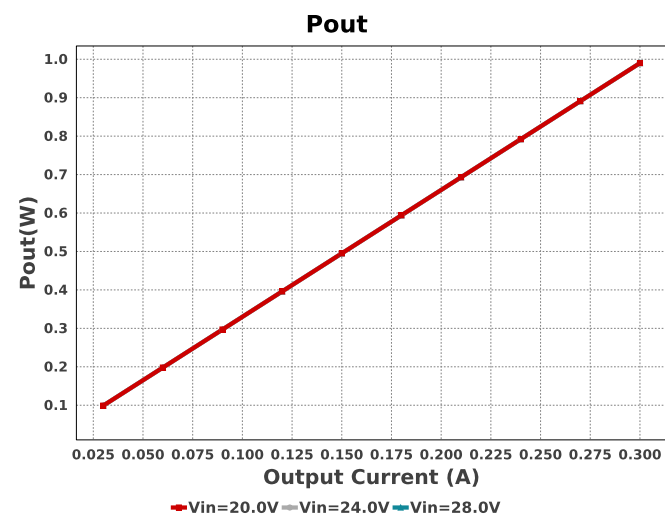

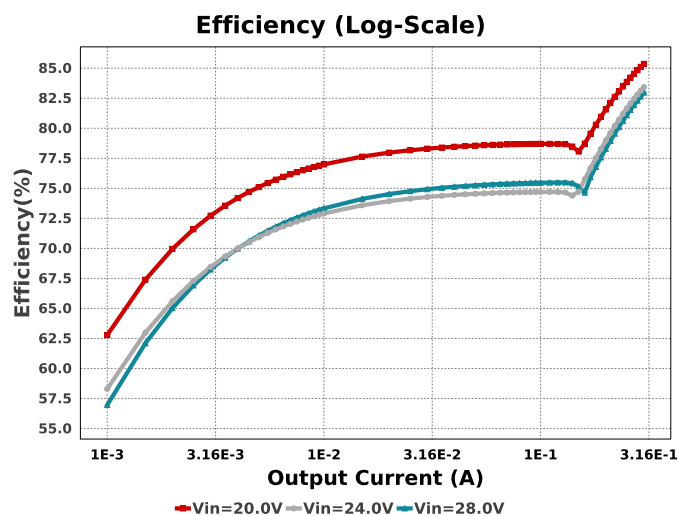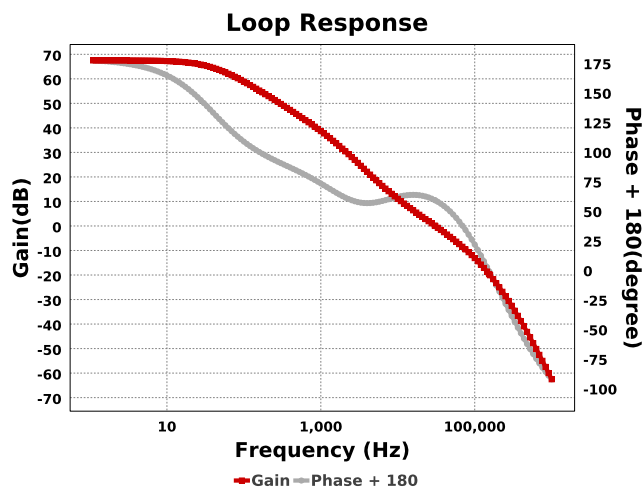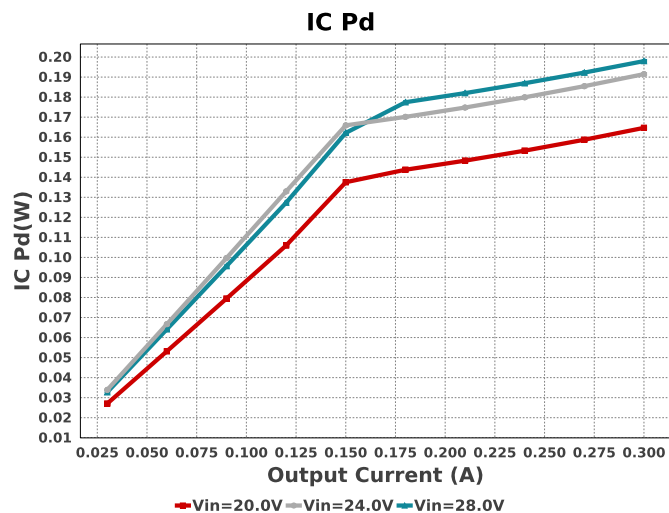

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	12		Total Design BOM count
2.	Total BOM	\$1.118		Total BOM Cost
3.	Cin IRMS	97.411 mA	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	28.466 μ W	Capacitor	Input capacitor power dissipation
5.	Cinx IRMS	3.112 mA	Capacitor	Bulk capacitor RMS ripple current
6.	Cinx Pd	9.685 nW	Capacitor	Bulk capacitor power dissipation
7.	Cout IRMS	65.106 mA	Capacitor	Output capacitor RMS ripple current
8.	Cout Pd	15.069 μ W	Capacitor	Output capacitor power dissipation
9.	IC Ipk	412.766 mA	IC	Peak switch current in IC
10.	IC Pd	197.98 mW	IC	IC power dissipation
11.	IC Tj	55.839 degC	IC	IC junction temperature
12.	IC Tolerance	20.0 mV	IC	IC Feedback Tolerance
13.	ICThetaJA Effective	80.0 degC/W	IC	Effective IC Junction-to-Ambient Thermal Resistance
14.	Iin Avg	42.612 mA	IC	Average input current
15.	Ipp percentage	75.177 %	Inductor	Inductor ripple current percentage (with respect to average inductor current)
16.	L Ipp	225.532 mA	Inductor	Peak-to-peak inductor ripple current
17.	L Pd	4.995 mW	Inductor	Inductor power dissipation
18.	Cin Pd	28.466 μ W	Power	Input capacitor power dissipation
19.	Cinx Pd	9.685 nW	Power	Bulk capacitor power dissipation
20.	Cout Pd	15.069 μ W	Power	Output capacitor power dissipation
21.	IC Pd	197.98 mW	Power	IC power dissipation
22.	L Pd	4.995 mW	Power	Inductor power dissipation
23.	Total Pd	203.143 mW	Power	Total Power Dissipation
24.	Cross Freq	30.73 kHz	System	Bode plot crossover frequency
25.	Duty Cycle	12.127 %	System Information	Duty cycle
26.	Efficiency	82.974 %	System Information	Steady state efficiency
27.	FootPrint	149.0 mm ²	System Information	Total Foot Print Area of BOM components

#	Name	Value	Category	Description
28.	Frequency	1.1 MHz	System Information	Switching frequency
29.	Gain Marg	-19.694 dB	System Information	Bode Plot Gain Margin
30.	Iout	300.0 mA	System Information	Iout operating point
31.	Low Freq Gain	67.505 dB	System Information	Gain at 1Hz
32.	Mode	CCM	System Information	Conduction Mode
33.	Phase Marg	60.077 deg	System Information	Bode Plot Phase Margin
34.	Pout	990.0 mW	System Information	Total output power
35.	Vin	28.0 V	System Information	Vin operating point
36.	Vin p-p	13.267 mV	System Information	Peak-to-peak input voltage
37.	Vout	3.3 V	System Information	Operational Output Voltage
38.	Vout Actual	3.327 V	System Information	Vout Actual calculated based on selected voltage divider resistors
39.	Vout Tolerance	4.073 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
40.	Vout p-p	2.278 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	300.0 m	Maximum Output Current
VinMax	28.0	Maximum input voltage
VinMin	20.0	Minimum input voltage
Vout	3.3	Output Voltage
base_pn	LMR54406	Base Product Number
source	DC	Input Source Type
Ta	40.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 20.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

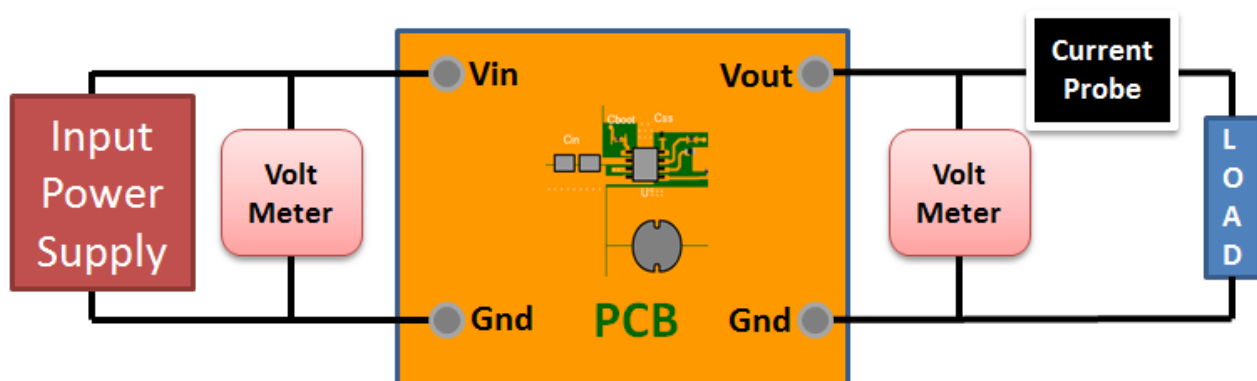

Design Assistance

1. Master key : 03B71B8129145358[v1]
2. **LMR54406** Product Folder : <http://www.ti.com/product/LMR54406> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with TI products.